

# MOSFETS LOGIC GATES

**Muhammad Adeel**


**M.Sc. Electronics (KU)**

**M.Phil. ISPA (KU)**
 
## CMOS (Complementary MOS)


CMOS combines n-channel and p-channel E-MOSFETs in a series arrangement. The input voltage at the gates is either 0 V or  $V_{DD}$ . Notice that  $V_{DD}$  and ground are both connected to source terminals of the transistors.

The term  $V_{DD}$  is used for the positive voltage, which is on the p-channel device's source terminal.




When  $V_{in} = 0\text{ V}$ ,  $Q_1$  is on and  $Q_2$  is off.

 Because  $Q_1$  is acting as a closed switch, the output is approximately  $V_{DD}$ .



When  $V_{in} = V_{DD}$ ,  $Q_2$  is on and  $Q_1$  is off,

 Because  $Q_2$  is acting as a closed switch, the output is essentially connected to ground ( $0\text{ V}$ ).



# Inverter



## Truth Table

$V_{IN}$	$V_{OUT}$
High	Low
Low	High

A	B
0	1
1	0

## NOT


A	B
0	1
1	0

  

# NAND

$V_A$	$V_B$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$V_{out}$
0	0	on	off	off	on	$V_{DD}$
0	$V_{DD}$	off	off	on	on	$V_{DD}$
$V_{DD}$	0	on	on	off	off	$V_{DD}$
$V_{DD}$	$V_{DD}$	off	on	on	off	0


 
When  $V_A$  and  $V_B$  are high, the output is low; otherwise, the output is high.



# NAND


## NAND

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

  

# NOR



$V_A$	$V_B$	$Q_1$	$Q_2$	$Q_3$	$Q_4$	$V_{out}$
0	0	on	off	on	off	$V_{DD}$
0	$V_{DD}$	off	on	on	off	0
$V_{DD}$	0	on	off	on	off	0
$V_{DD}$	$V_{DD}$	off	on	off	on	0

 

# NOR

## NOR

A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

  





# AND

## AND


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

 

May you draw the circuit now....?

 


# AND

 


OR

OR

A B		C
0	0	0
0	1	1
1	0	1
1	1	1

 

May you draw the circuit now....?

 

OR

