

# Operational Amplifiers

**Muhammad Adeel**

**M.Sc. Electronics (KU)**

**M.Phil. ISPA (KU)**

Early operational amplifiers (op-amps) were used primarily to perform mathematical operations such as,

**Addition**

**Subtraction**

**Integration**


**Differentiation**

thus the term **operational**.

These early devices were constructed with vacuum tubes and worked with high voltages.

Today's op-amps are linear integrated circuits (ICs) that use relatively low dc supply voltages and are reliable and inexpensive.

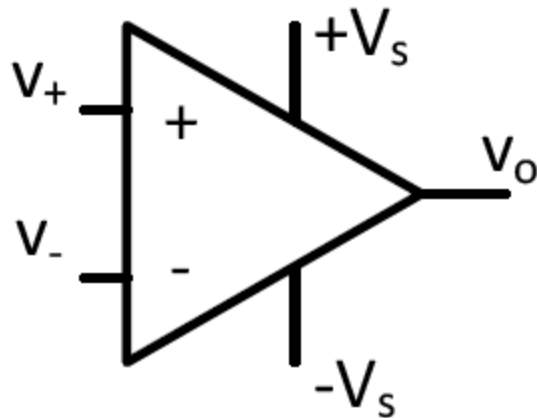Specialized circuit made up of transistors, resistors, and capacitors fabricated on an integrated chip




### Uses:

- Amplifiers
- Active Filters
- Analog Computers
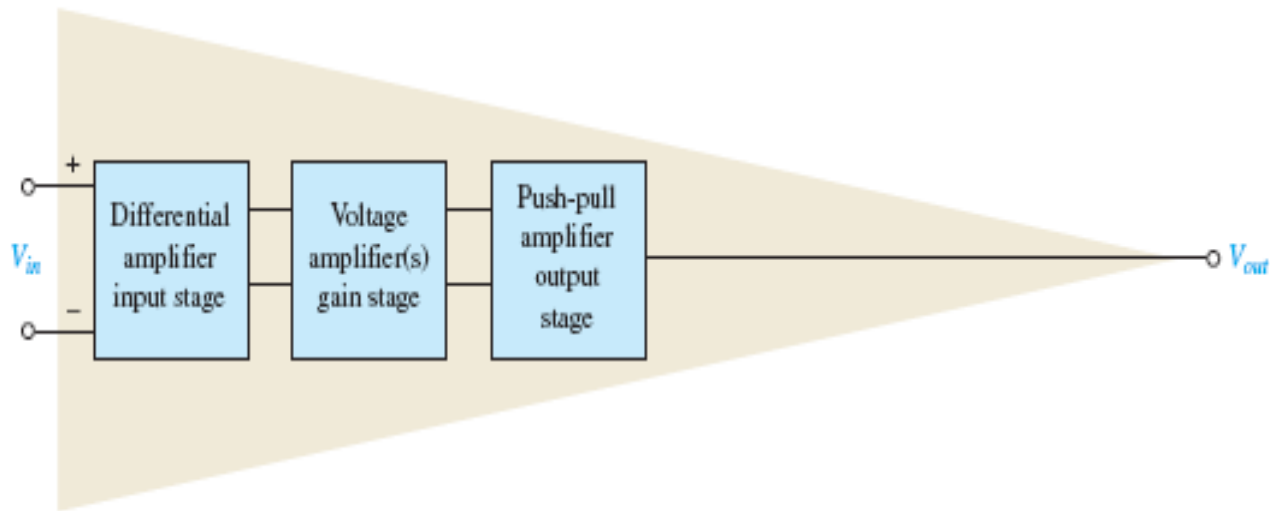
# The Practical Op-Amp



Characteristics of a practical op-amp are  
**very high voltage gain,**  
**very high input impedance,** and  
**very low output impedance.**



## Op-Amps in Circuits

- Active Element: has its own power supply
- Symbol ignores the  $\pm V_s$  in the symbol since it does not affect circuit behavior


Symbol:

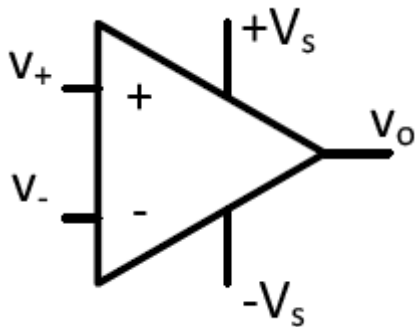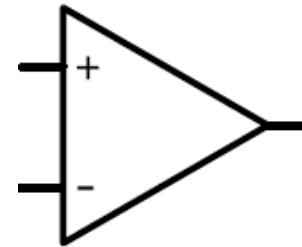


$V_s = 10V, 15V$

Signal	PIN
$v_-$	2
$v_+$	3
$-V_s$	4
$v_o$	6
$+V_s$	7

## Open Loop Behavior

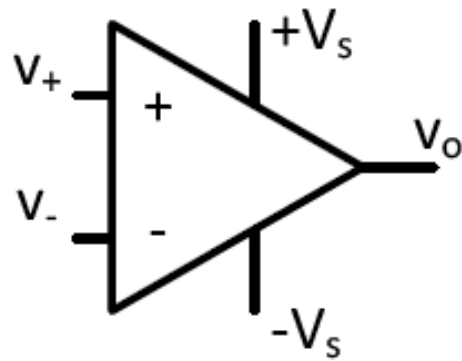

$$v_o = A(v_+ - v_-)$$

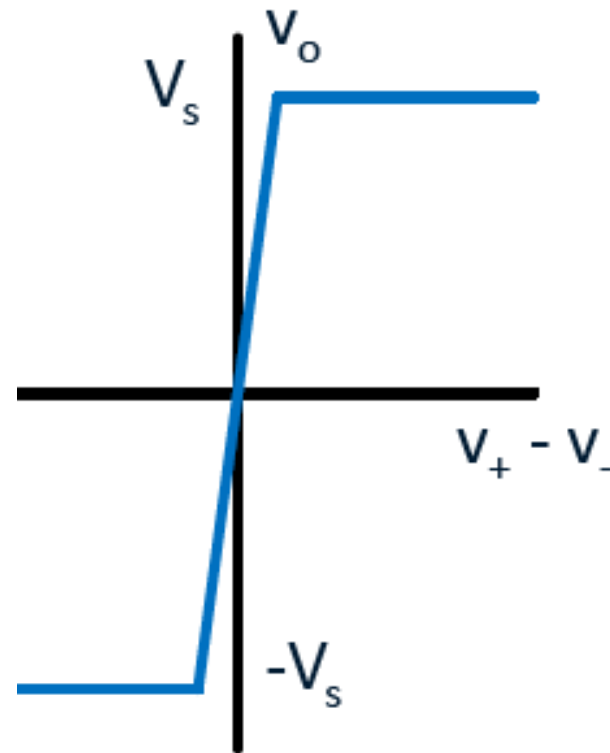

The inherent open-loop voltage gain of a typical op-amp is very high (usually greater than 100,000).

Therefore, an extremely small input voltage drives the op-amp into its saturated output states.


In fact, even the input offset voltage of the op-amp can drive it into saturation.

For example, assume  $V_{IN} = 1 \text{ mV}$  and  $A_{ol} = 100,000$ .


Then,

$$V_{IN}A_{ol} = (1 \text{ mV})(100,000) = 100 \text{ V}$$

## Comparator Circuit


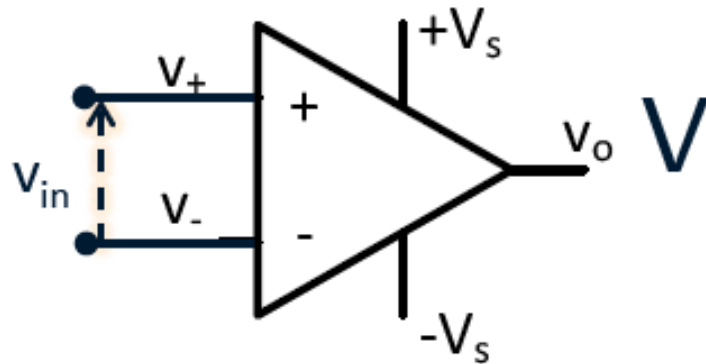

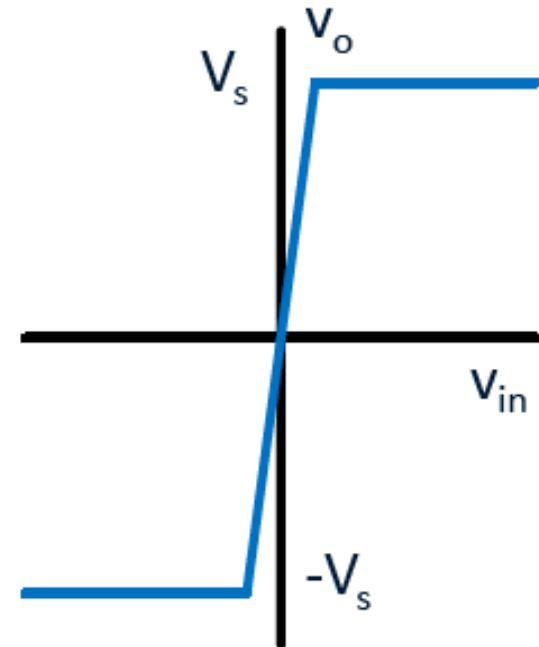
$$V_o = \begin{cases} V_s & \text{if } v_{in} > 0 \\ -V_s & \text{if } v_{in} < 0 \end{cases}$$





## Ideal Op-Amp Behavior

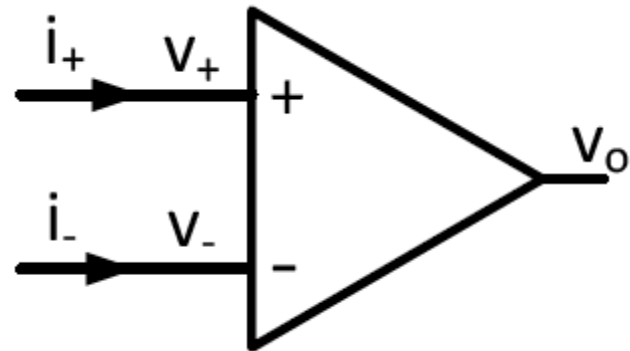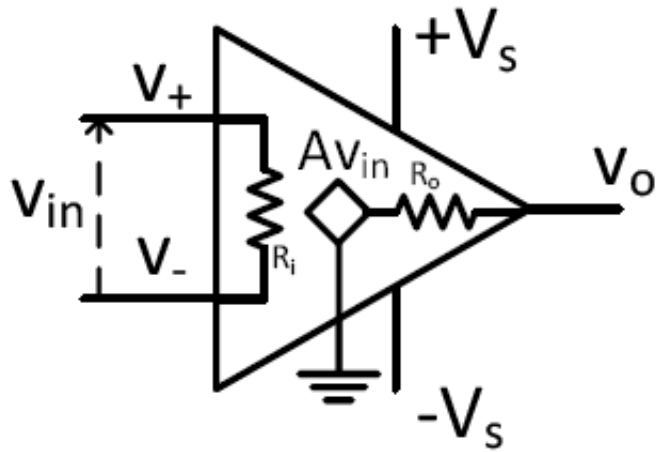


$$i_+ = i_- = 0$$

$$v_+ - v_- = 0$$


# Negative Feedback
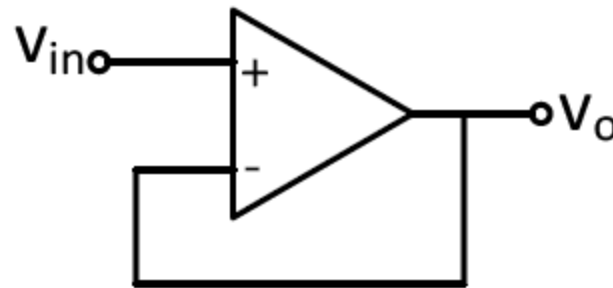
## Buffer circuit


Use to boost the power without changing the voltage waveform.




$$V_{in} = V_o$$

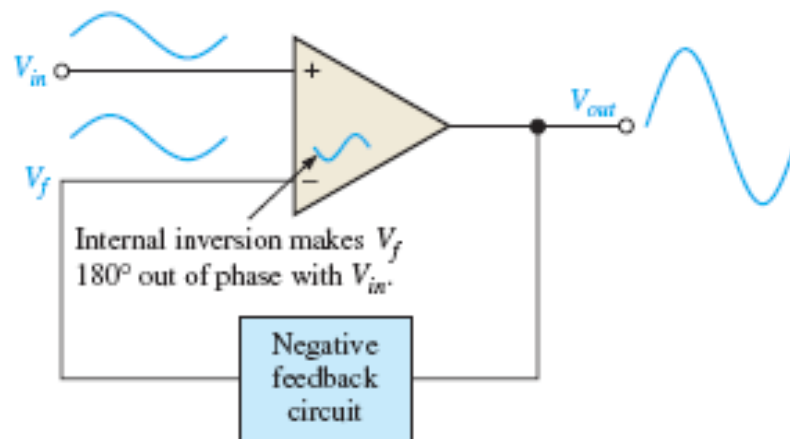


# Differentiator Circuit

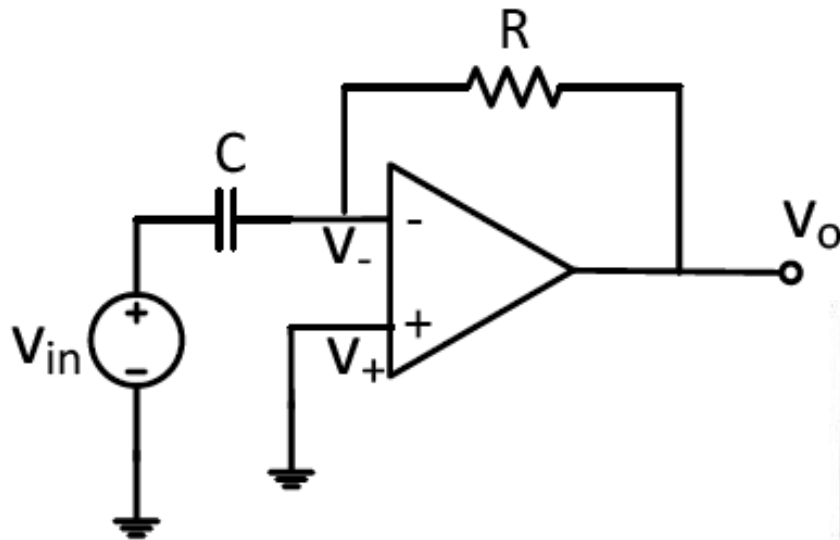

$$V_o = -RC \frac{dV_{in}}{dt}$$

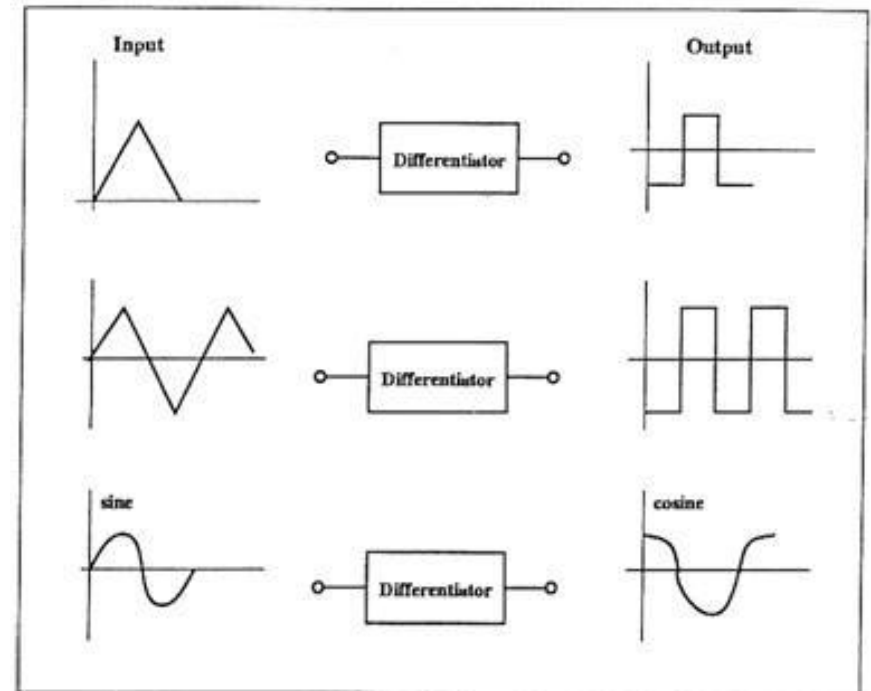

# Integrator Circuit

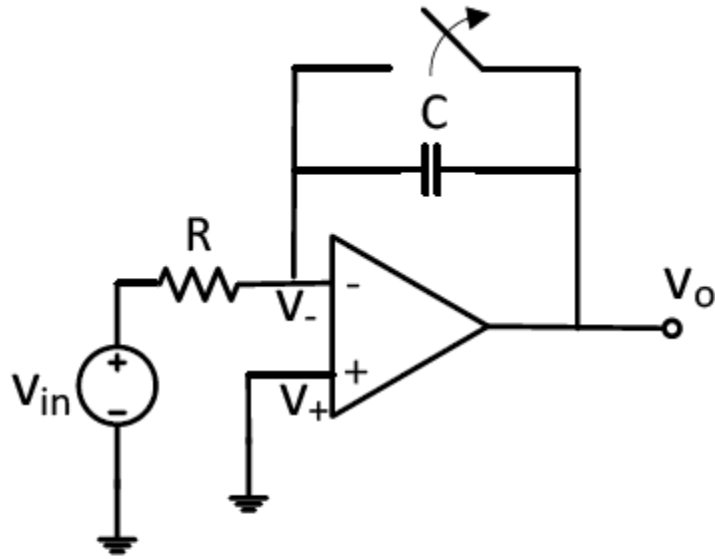

$$V_o = -\frac{1}{RC} \int_0^t V_{in} dt$$

