

# Class B Power Amplifier


**Muhammad Adeel**

**M.Sc. Electronics (KU)**

**M.Phil. ISPA (KU)**
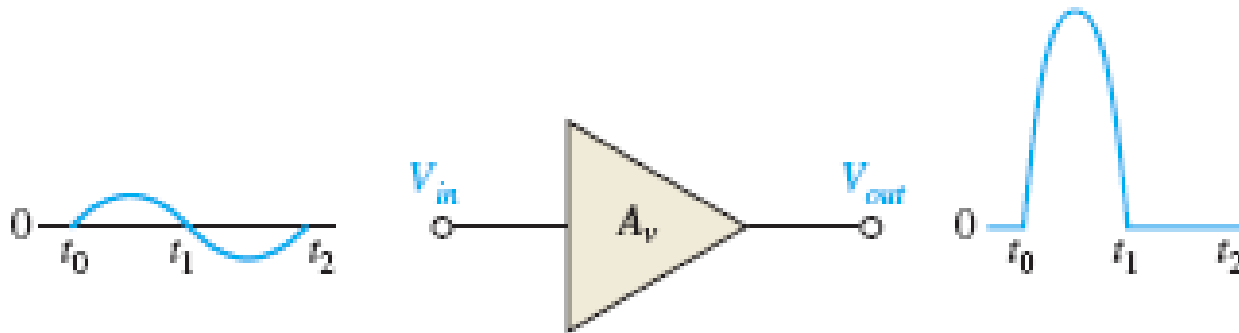
# Class B Power Amplifier


When an amplifier is biased at cutoff so that it operates in the linear region for of the input cycle and is in cutoff for it is a **class B amplifier**.


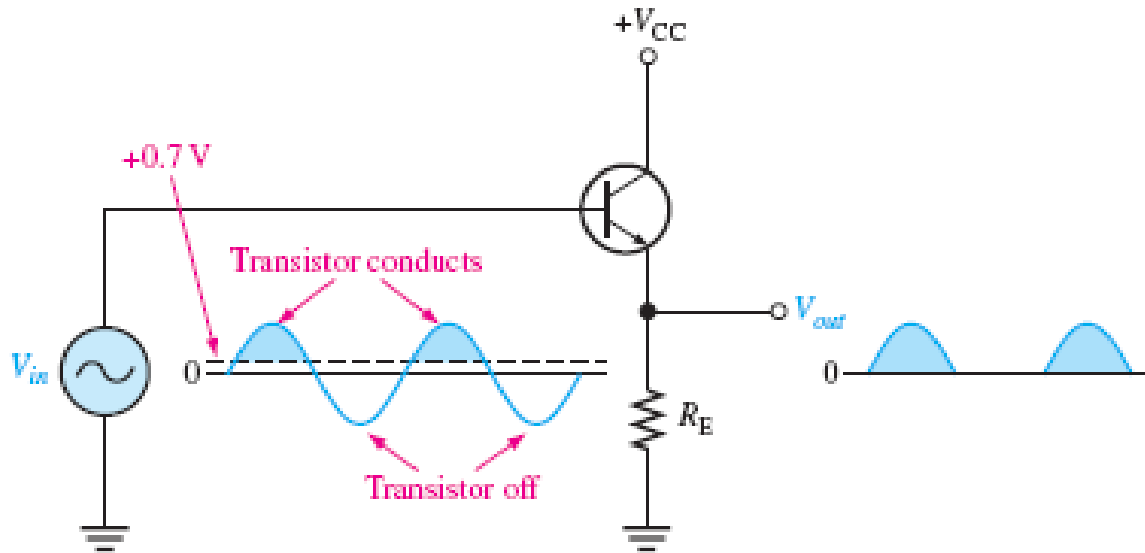
## The Q-Point is at Cutoff

The class B amplifier is biased at the cutoff point so that  $I_{CQ} = 0$  and  $V_{CEQ} = V_{CE(\text{cutoff})}$ .

It is brought out of cutoff and operates in its linear region when the input signal drives the transistor into conduction.



## Class B Push Pull Amplifier


To amplify the entire cycle, it is necessary to add a second class B amplifier that operates on the negative half of the cycle.

The combination of two class B amplifiers working together is called **push-pull operation**.


There are two common approaches for using push-pull amplifiers to reproduce the entire waveform. The first approach uses transformer coupling.

The second uses two **complementary symmetry transistors**; these are a **matching pair of *npn/pnp BJT***


# Transformer Coupling

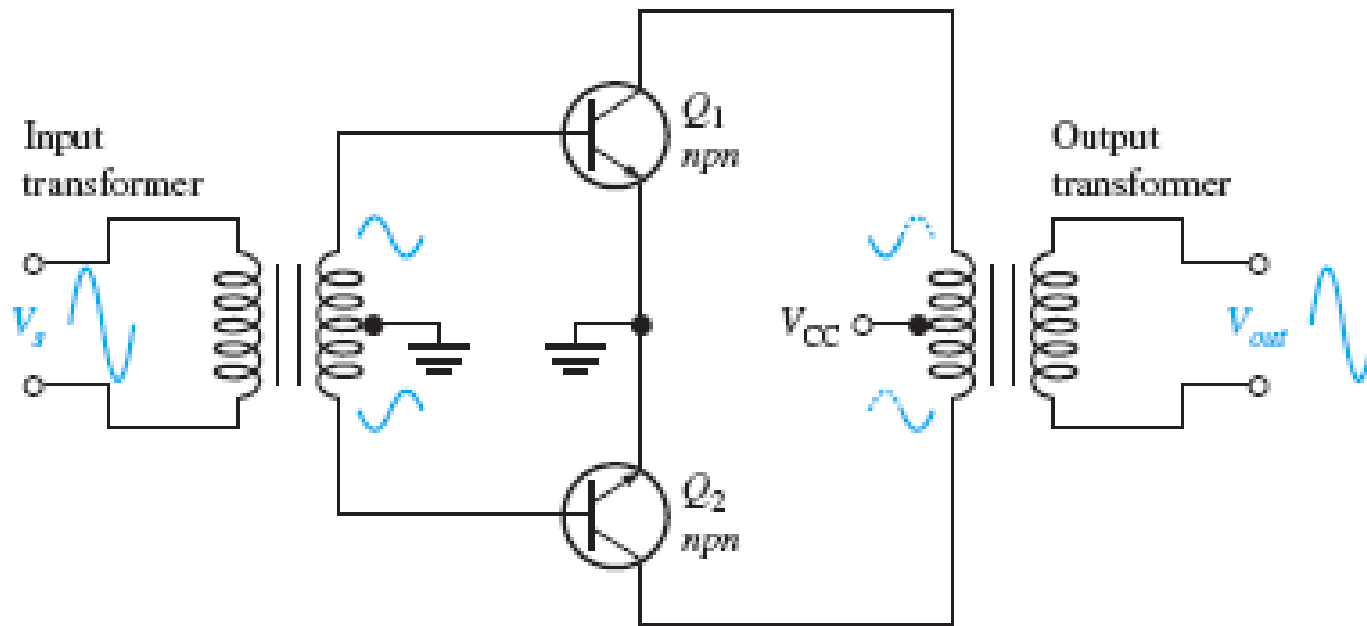

# Complementary Symmetry Transistors

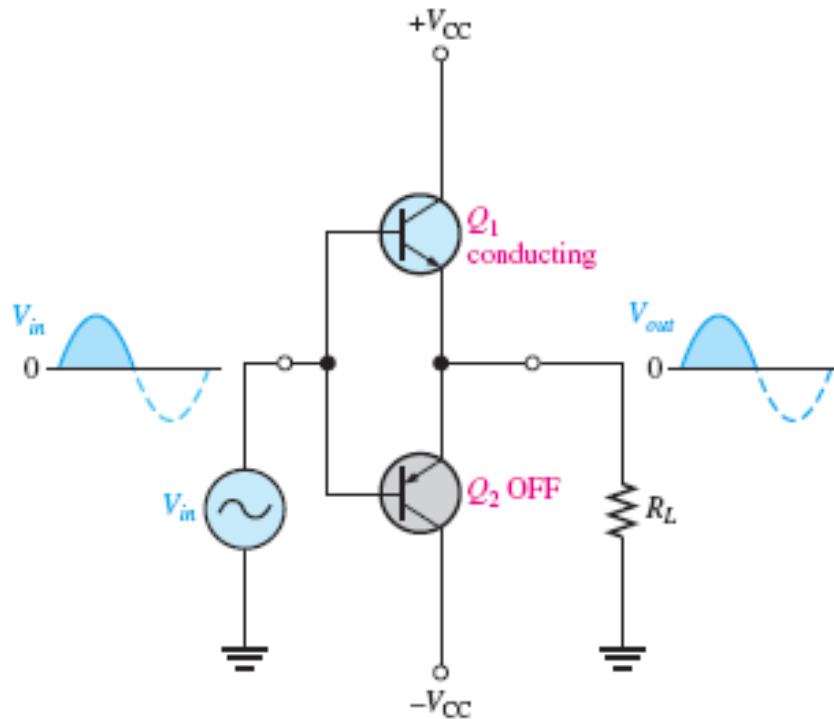


(a) During a positive half-cycle

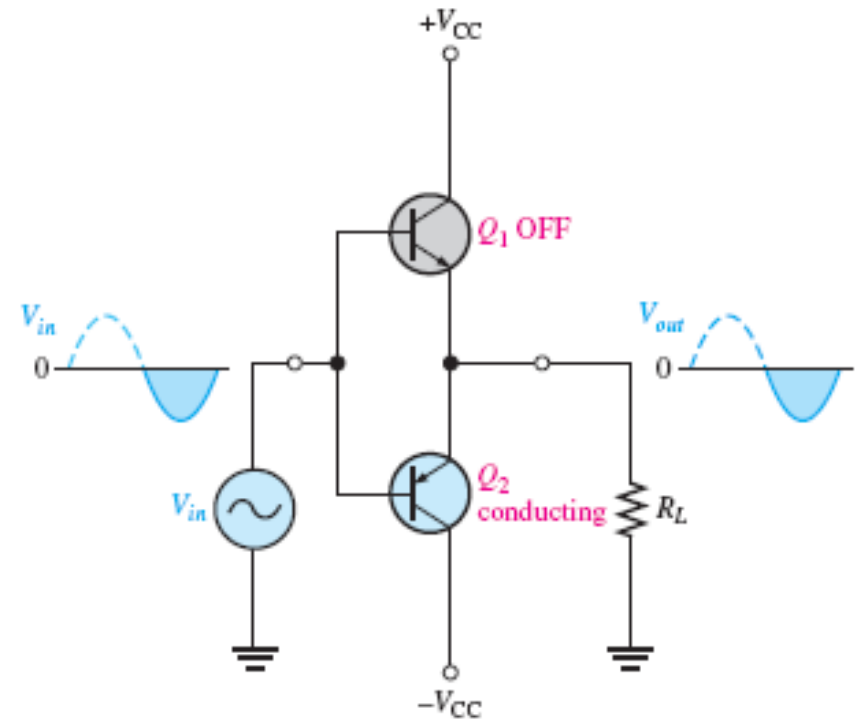

(b) During a negative half-cycle

## Crossover Distortion

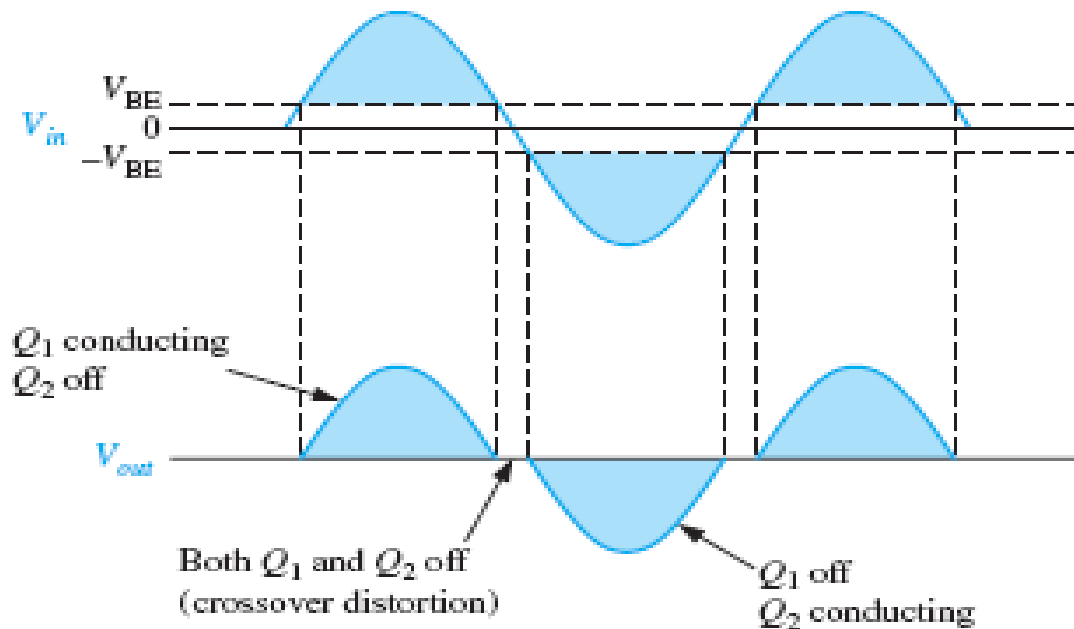

When the dc base voltage is zero, both transistors are off and the input signal voltage must exceed  $V_{BE}$  before a transistor conducts.


*Because of this, there is a time interval between the positive and negative alternations of the input when neither transistor is conducting, as shown in Figure.*

The resulting distortion in the output waveform is called **crossover distortion**.
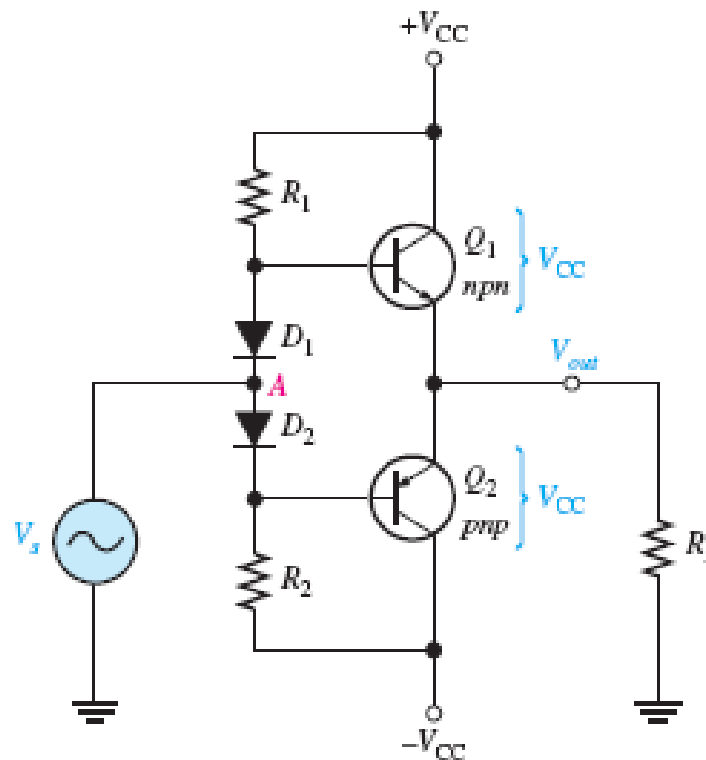
## Method to Eliminate Crossover Distortion

To overcome crossover distortion, the biasing is adjusted to just overcome the  $V_{BE}$  of the transistors; this results in a modified form of operation called **class AB**. In **class AB operation**, the push-pull stages are biased into slight conduction, even when no input signal is present.


This can be done with a voltage-divider and diode arrangement,






$$I_{CQ} = \frac{V_{CC} - 0.7 \text{ V}}{R_1}$$

$$I_{c(sat)} = \frac{V_{CC}}{R_L}$$

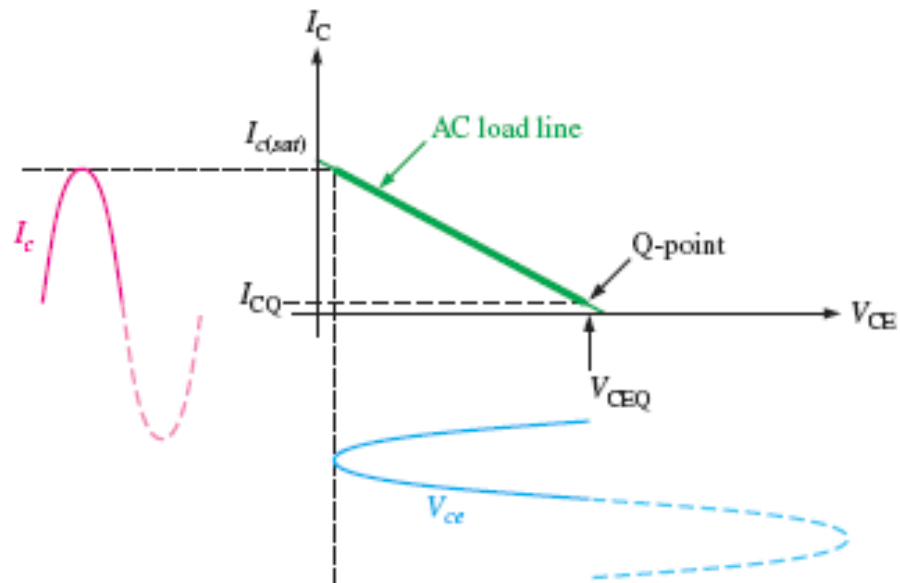

(a) AC load line for  $Q_1$

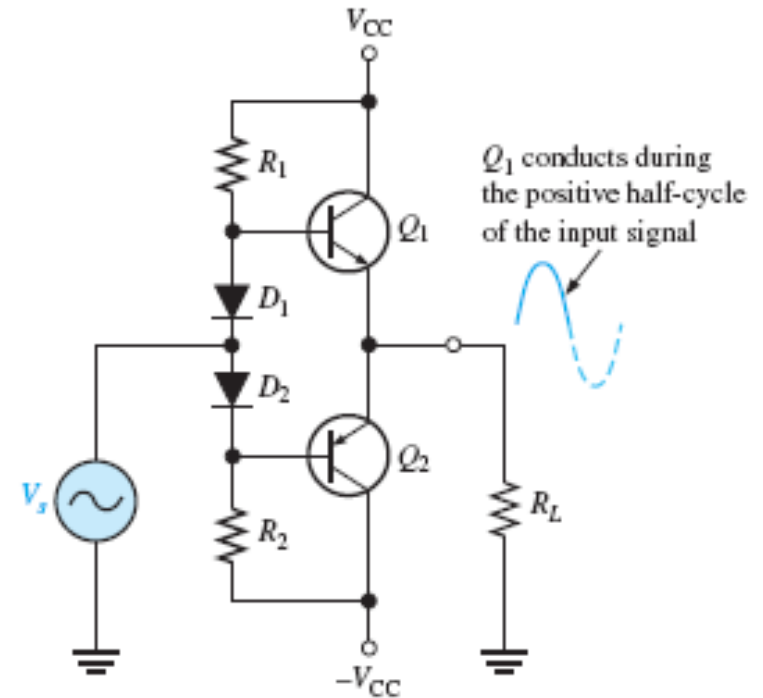


(b) Circuit

## Example

Determine the ideal maximum peak output voltage and current for the circuit shown in Figure.

The ideal maximum peak output voltage is
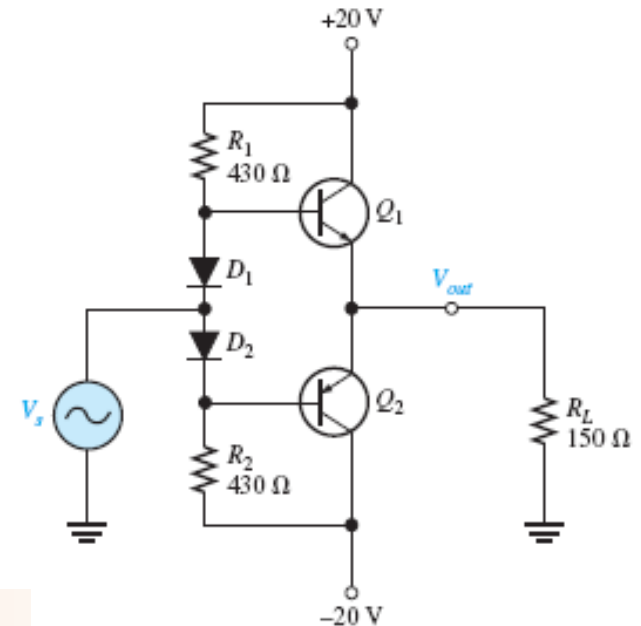
$$V_{out(peak)} \cong V_{CEQ} \cong V_{CC} = 20 \text{ V}$$



The ideal maximum peak current is

$$I_{out(peak)} \cong I_{c(sat)} \cong \frac{V_{CC}}{R_L} = \frac{20 \text{ V}}{150 \Omega} = 133 \text{ mA}$$

The actual maximum values of voltage and current are slightly smaller.

## Class B/AB Power

**Maximum Output Power** You have seen that the ideal maximum peak output current for both dual-supply and single-supply push-pull amplifiers is approximately  $I_{c(sat)}$ , and the maximum peak output voltage is approximately  $V_{CEQ}$ . Ideally, the maximum *average* output power is, therefore,

$$P_{out} = I_{out(rms)} V_{out(rms)}$$

Since

$$I_{out(rms)} = 0.707 I_{out(peak)} = 0.707 I_{c(sat)}$$

and

$$V_{out(rms)} = 0.707 V_{out(peak)} = 0.707 V_{CEQ}$$

then

$$P_{out} = 0.5 I_{c(sat)} V_{CEQ}$$

Substituting  $V_{CC}/2$  for  $V_{CEQ}$ , the maximum average output power is

$$P_{out} = 0.25 I_{c(sat)} V_{CC}$$

**DC Input Power** The dc input power comes from the  $V_{CC}$  supply and is

$$P_{DC} = I_{CC}V_{CC}$$

Since each transistor draws current for a half-cycle, the current is a half-wave signal with an average value of

$$I_{CC} = \frac{I_{c(sat)}}{\pi}$$

So,

$$P_{DC} = \frac{I_{c(sat)}V_{CC}}{\pi}$$

**Efficiency** An advantage of push-pull class B and class AB amplifiers over class A is a much higher efficiency. This advantage usually overrides the difficulty of biasing the class AB push-pull amplifier to eliminate crossover distortion. Recall that efficiency,  $\eta$  is defined as the ratio of ac output power to dc input power.

$$\eta = \frac{P_{out}}{P_{DC}}$$

The maximum efficiency,  $\eta_{max}$ , for a class B amplifier (class AB is slightly less) is developed as follows, starting with Equation 7-6.

$$\begin{aligned} P_{out} &= 0.25I_{c(sat)}V_{CC} \\ \eta_{max} &= \frac{P_{out}}{P_{DC}} = \frac{0.25I_{c(sat)}V_{CC}}{I_{c(sat)}V_{CC}/\pi} = 0.25\pi \\ \eta_{max} &= 0.79 \end{aligned}$$

or, as a percentage,

$$\eta_{max} = 79\%$$

Recall that the maximum efficiency for class A is 0.25 (25 percent).

## Input Resistance

The complementary push-pull configuration used in class B/class AB amplifiers is, in effect, two emitter-followers. The input resistance for the emitter-follower, where  $R_1$  and  $R_2$  are the bias resistors, is

$$R_{in} = \beta_{ac}(r'_e + R_E) \parallel R_1 \parallel R_2$$

Since  $R_E = R_L$ , the formula is

$$R_{in} = \beta_{ac}(r'_e + R_L) \parallel R_1 \parallel R_2$$