

# Biased Clippers and Clampers

**Muhammad Adeel**



**M.Sc. Electronics (KU)**

**M.Phil. ISPA (KU)**



## **BIASED LIMITERS:**

- The level to which an AC signal is limited can be adjusted by adding a bias voltage  $V_{BIAS}$ , in series with the diode in the circuit.
- The series combination of the diode and the bias voltage determines which portion of the input signal will be allowed to appear at the output.



## Positive Biased Limiters:

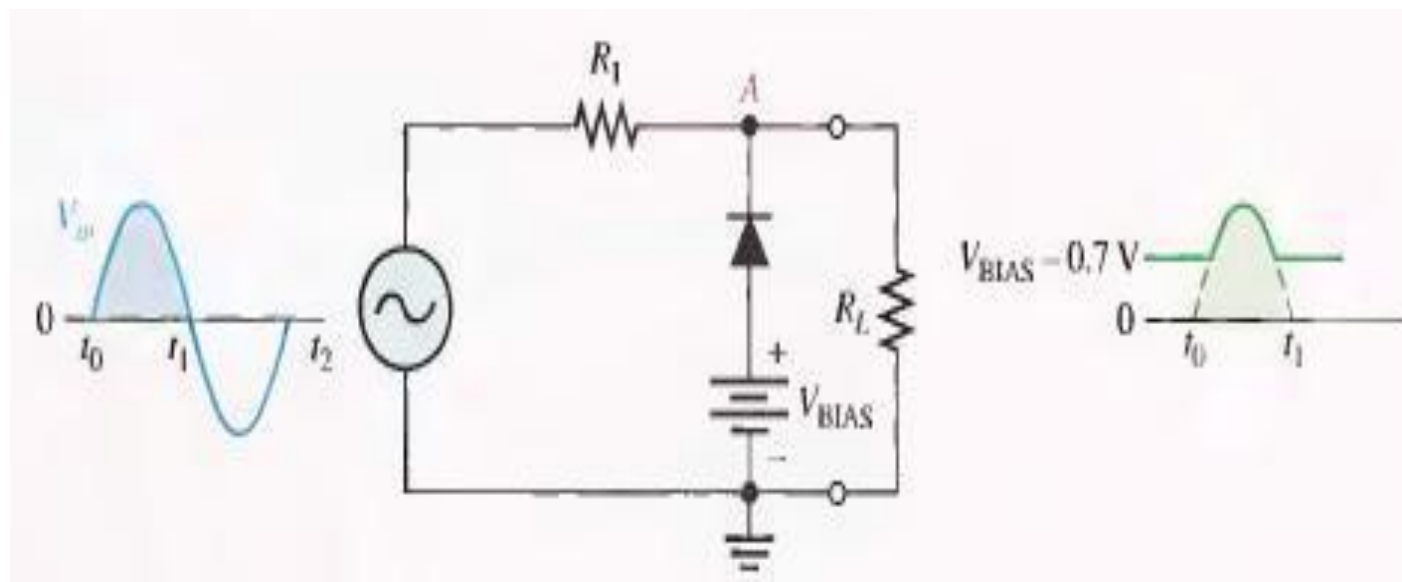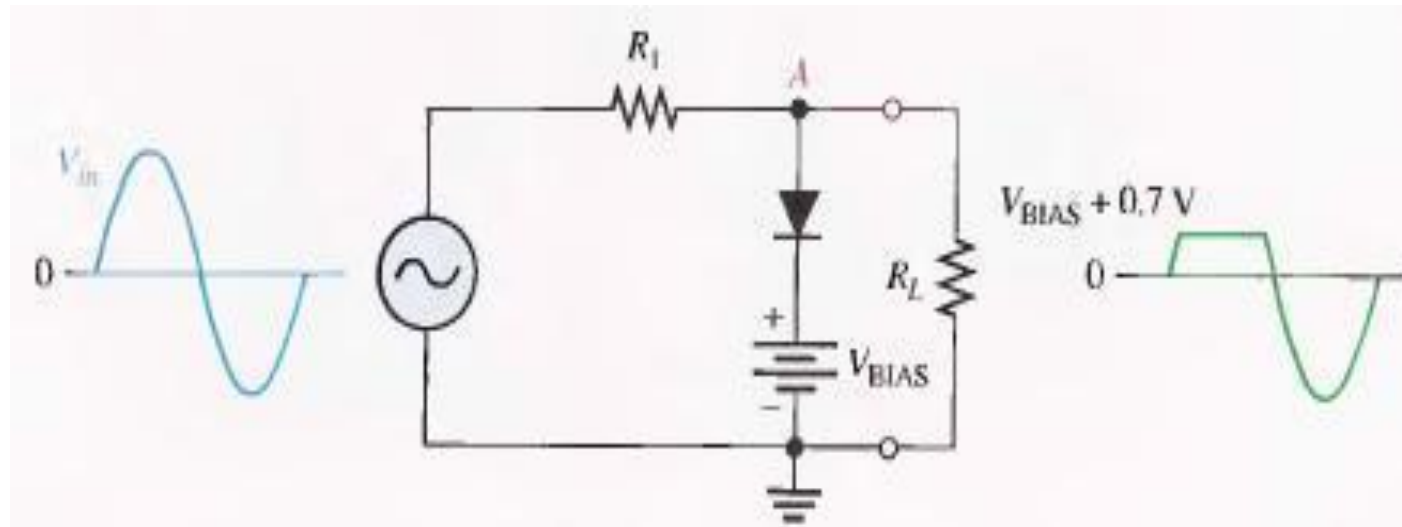


## Negative Biased Limiters:

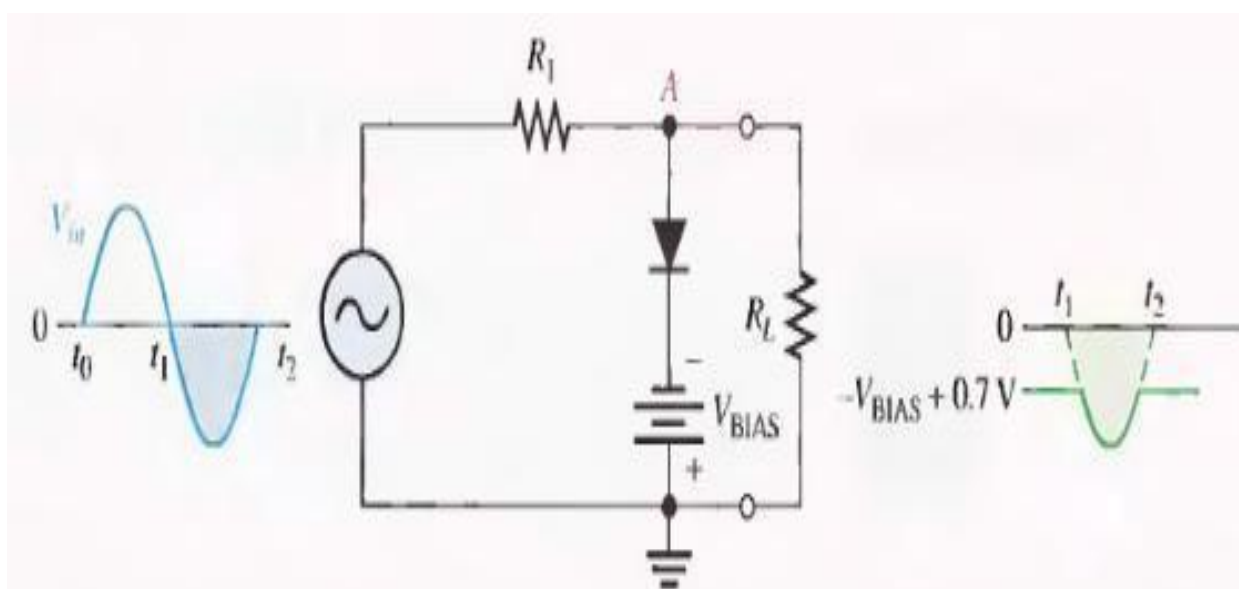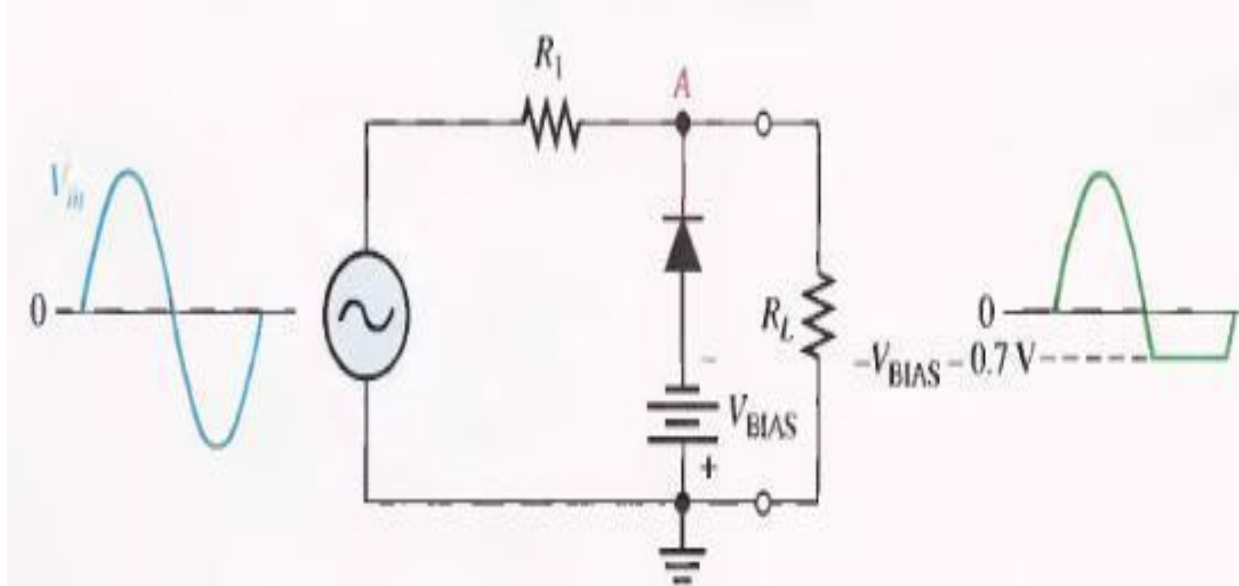

## Example:

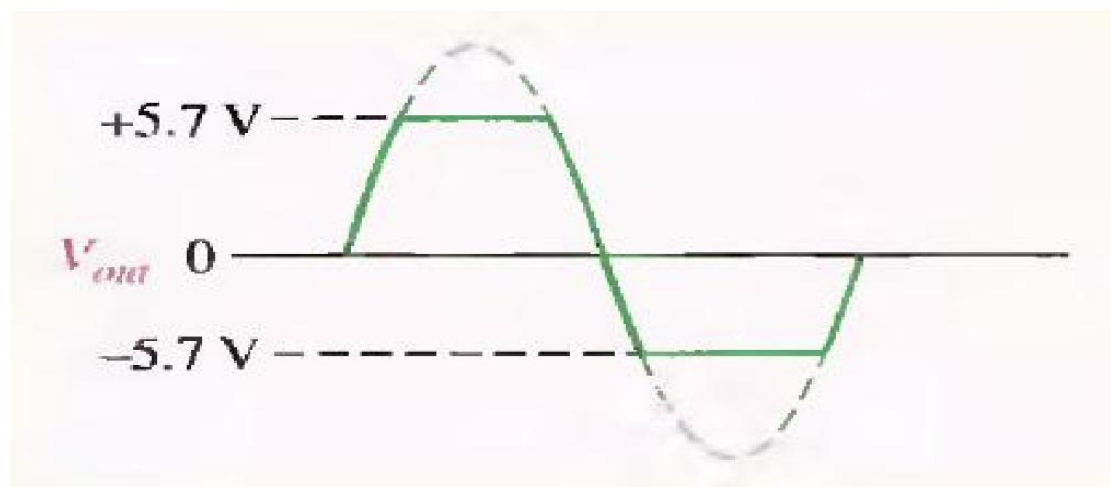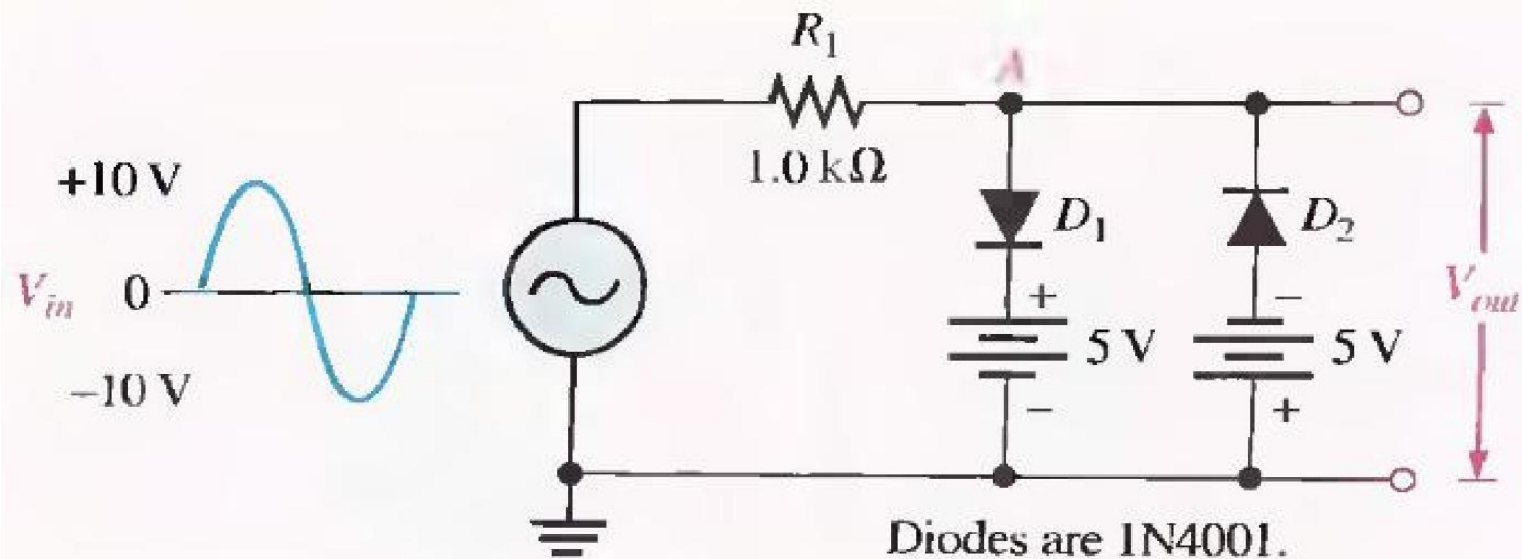


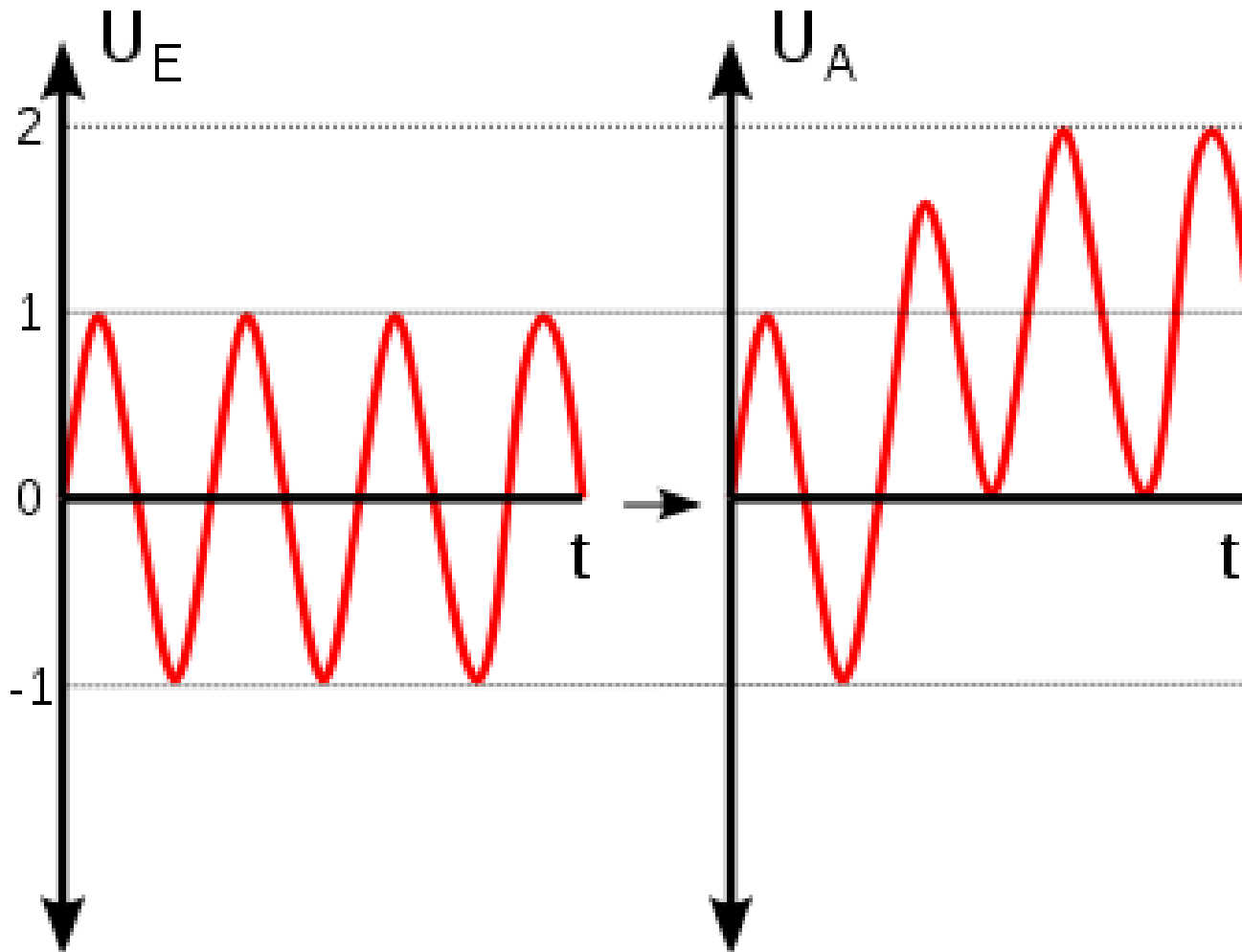

# DIODE CLAMPERS:

➤ Diode Clamper circuits are used to add or restore a DC level to an electrical AC signal.


## Positive Clampers:

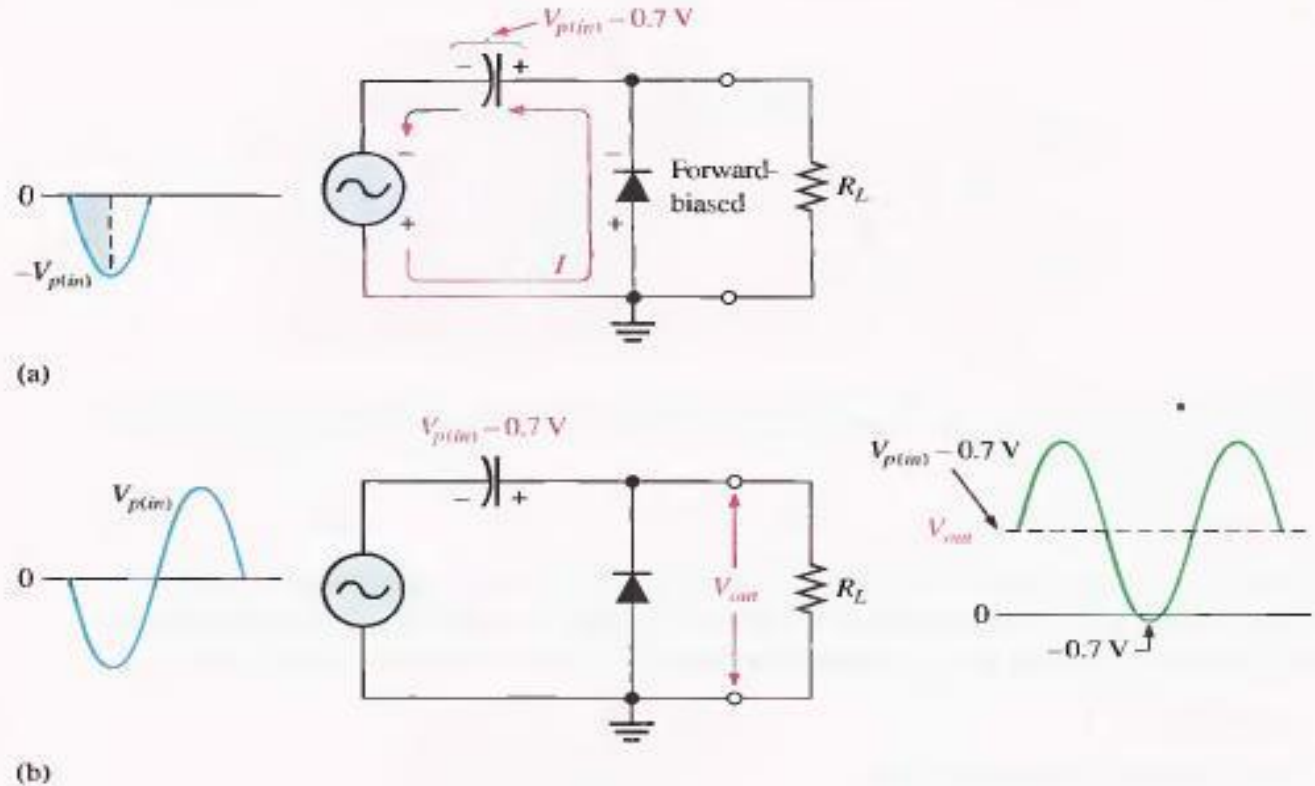

The net effect of the clamping action is that the capacitor retains a charge approximately equal to the peak value of the input less the diode drop. The capacitor voltage acts essentially as a battery in series with the input voltage. The dc voltage of the capacitor adds to the input voltage by superposition, as in Figure 2-45(b).

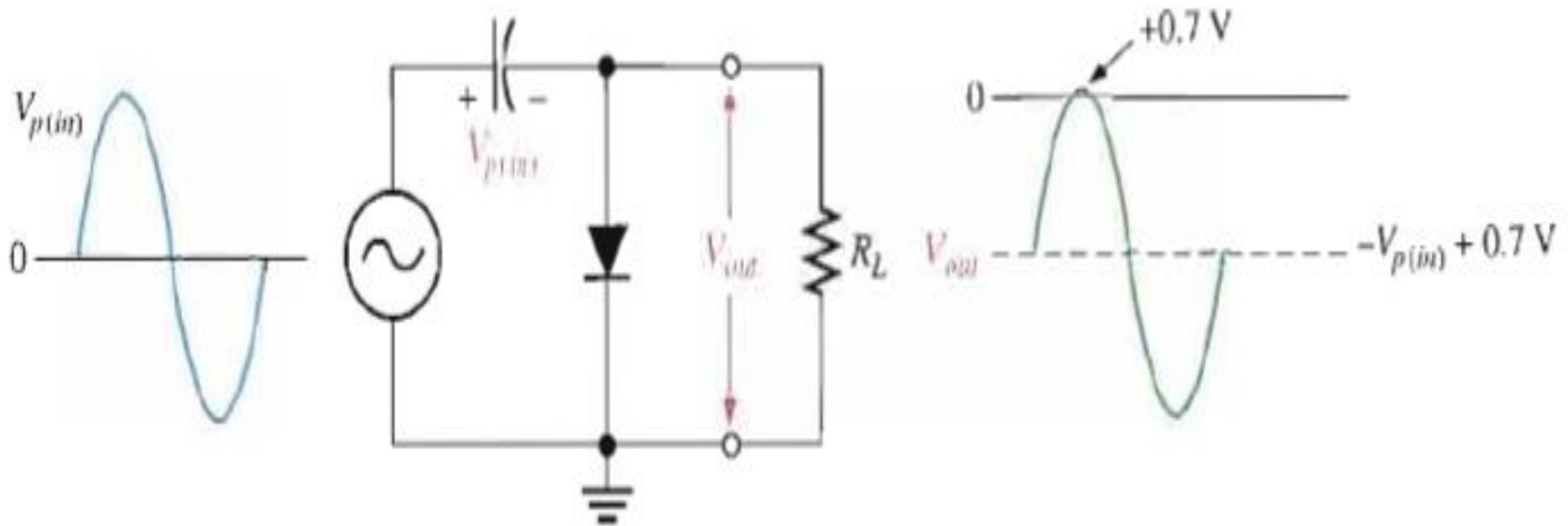
## Negative Clampers:

If the diode is turned around, a negative dc voltage is added to the input voltage to produce the output voltage as shown in Figure 2-46.





## Example:

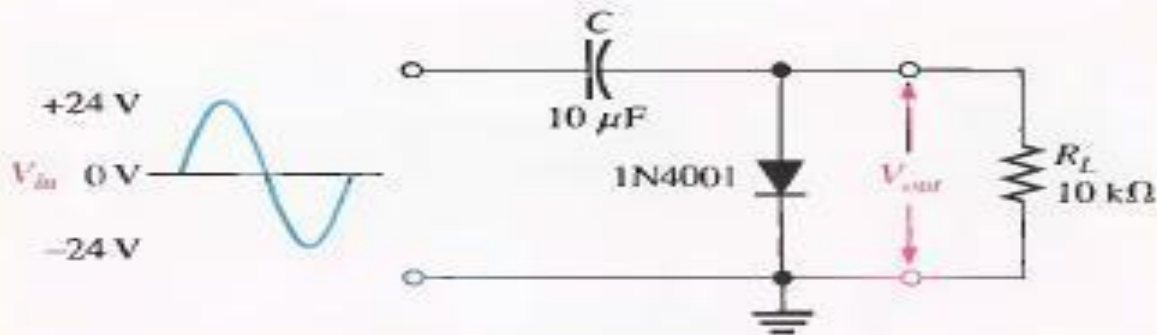

Ideally, a negative dc value equal to the input peak less the diode drop is inserted by the clamping circuit.

$$V_{DC} \equiv -(V_{p(in)} - 0.7\text{ V}) = -(24\text{ V} - 0.7\text{ V}) = -23.3\text{ V}$$

Actually, the capacitor will discharge slightly between peaks, and, as a result, the output voltage will have an average value of slightly less than that calculated above. The output waveform goes to approximately  $+0.7\text{ V}$ , as shown in Figure 2-48.

**FIGURE 2-48**

Output waveform across  $R_L$  for Figure 2-47.

