

# Common Collector Amplifier

**Muhammad Adeel**

**M.Sc. Electronics (KU)**


**M.Phil. ISPA (KU)**

## THE COMMON-COLLECTOR (CC) AMPLIFIER

The common-collector (CC) amplifier is usually referred to as an emitter-follower (EF).

The input is applied to the base through a coupling capacitor, and the output is at the emitter.

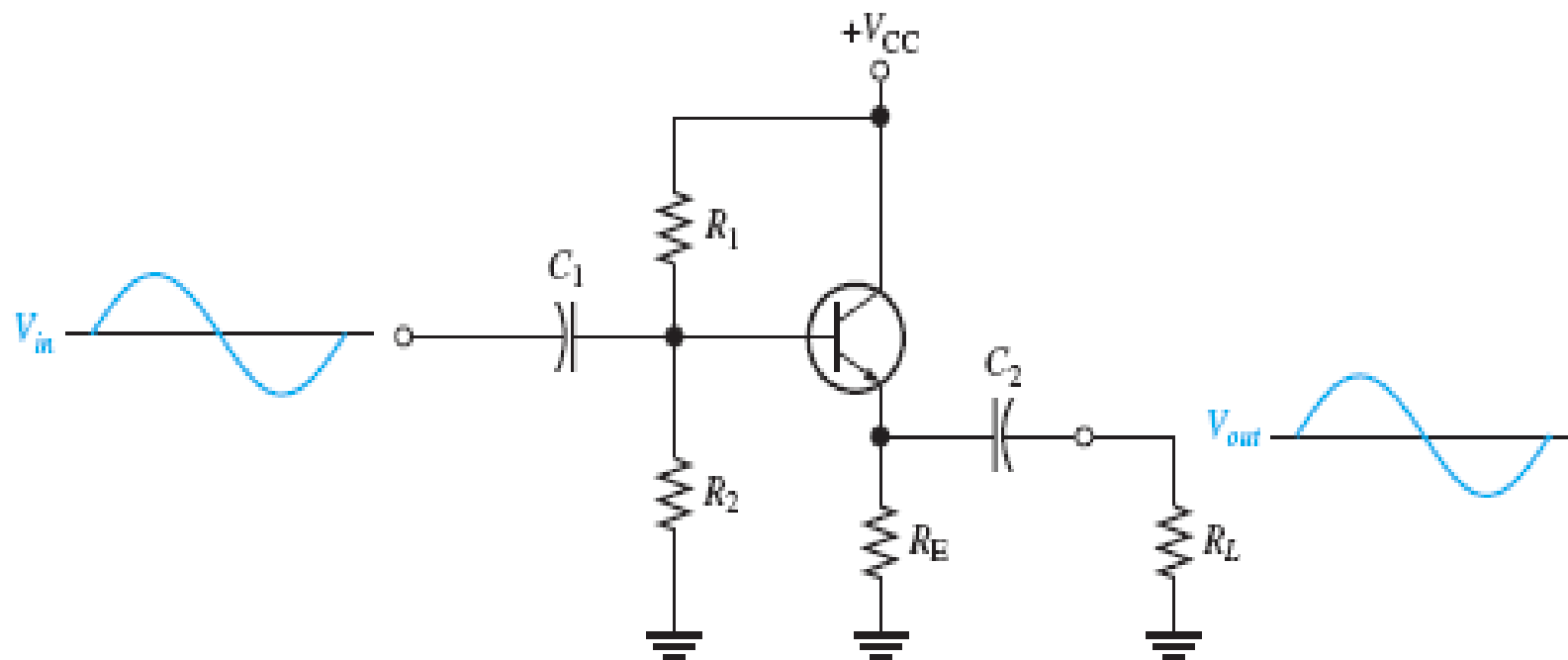The voltage gain of a CC amplifier is approximately 1, and its main advantages are its high input resistance and current gain.



## Voltage Gain


$$A_v = V_{out} / V_{in}$$

$$V_{out} = I_e R_e$$

$$V_{in} = I_e(r'_e + R_e)$$

$$A_v = \frac{I_e R_e}{I_e(r'_e + R_e)}$$

$$A_v = \frac{R_e}{r'_e + R_e}$$

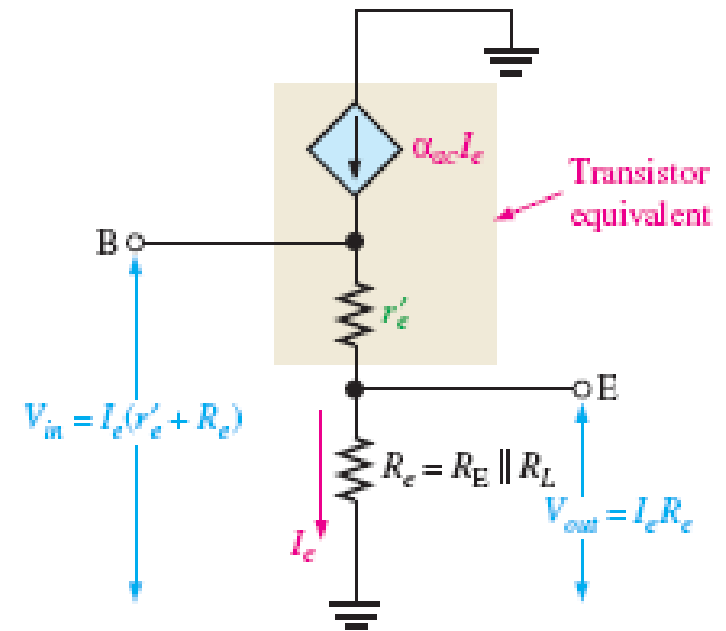

where  $R_e$  is the parallel combination of  $R_E$  and  $R_L$ . If there is no load, then  $R_e = R_E$ .

Notice that the gain is always less than 1.

If  $R_e \gg r'_e$ , then a good approximation is

$$A_v \cong 1$$

## Input Resistance

The emitter-follower is characterized by a high input resistance; this is what makes it a useful circuit. Because of the high input resistance, it can be used as a buffer to minimize loading effects when a circuit is driving a low-resistance load. The derivation of the input resistance, looking in at the base of the common-collector amplifier, is similar to that for the common-emitter amplifier. In a common-collector circuit, however, the emitter resistor is *never* bypassed because the output is taken across  $R_e$ , which is  $R_E$  in parallel with  $R_L$ .

$$R_{in(base)} = \frac{V_{in}}{I_{in}} = \frac{V_b}{I_b} = \frac{I_e(r'_e + R_e)}{I_b}$$

Since  $I_e \cong I_c = \beta_{ac} I_b$ ,

$$R_{in(base)} \cong \frac{\beta_{ac} I_b (r'_e + R_e)}{I_b}$$

The  $I_b$  terms cancel; therefore,

$$R_{in(base)} \cong \beta_{ac} (r'_e + R_e)$$

If  $R_e \gg r'_e$ , then the input resistance at the base is simplified to

$$R_{in(base)} \cong \beta_{ac} R_e$$

The bias resistors in Figure 6–25 appear in parallel with  $R_{in(base)}$ , looking from the input source; and just as in the common-emitter circuit, the total input resistance is

$$R_{in(tot)} = R_1 \parallel R_2 \parallel R_{in(base)}$$

## Output Resistance

With the load removed, the output resistance, looking into the emitter of the emitter-follower, is approximated as follows:

$$R_{out} \cong \left( \frac{R_s}{\beta_{ac}} \right) \parallel R_E$$

$R_s$  is the resistance of the input source. The derivation of Equation 6–14, found in “Derivations of Selected Equations” at [www.pearsonhighered.com/floyd](http://www.pearsonhighered.com/floyd), is relatively involved and several assumptions have been made. The output resistance is very low, making the emitter-follower useful for driving low-resistance loads.

## Current Gain

$$A_i = \frac{I_e}{I_{in}}$$

where  $I_{in} = V_{in}/R_{in(tot)}$ .

## Power Gain

The common-collector power gain is the product of the voltage gain and the current gain. For the emitter-follower, the power gain is approximately equal to the current gain because the voltage gain is approximately 1.


$$A_p = A_v A_i$$

Since  $A_v \cong 1$ , the power gain is

$$A_p \cong A_i$$
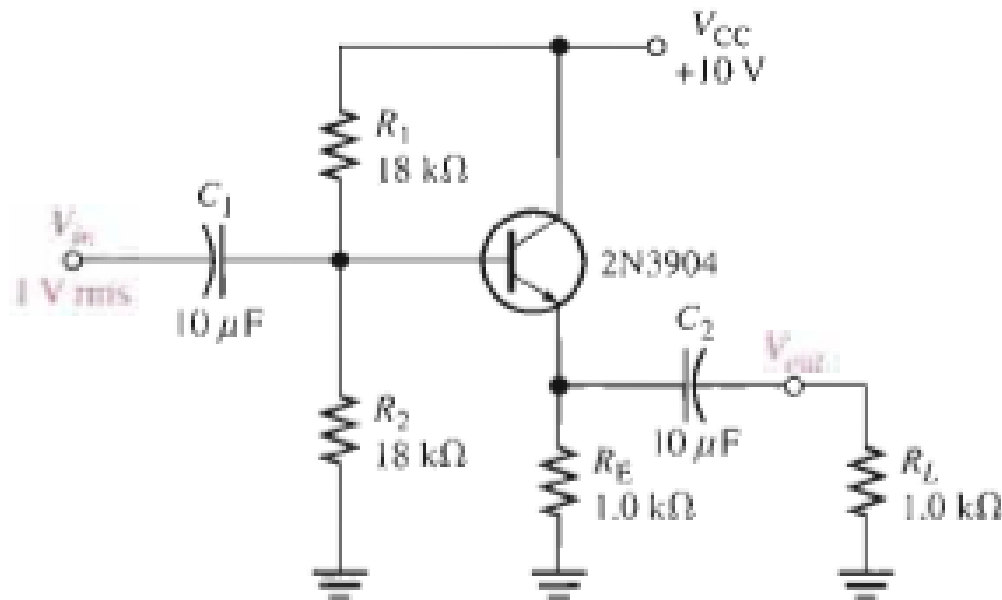
## Example

Determine the total input resistance of the emitter-follower in Figure 6–27. Also find the voltage gain, current gain, and power gain in terms of power delivered to the load,  $R_L$ . Assume  $\beta_{ac} = 175$  and that the capacitive reactances are negligible at the frequency of operation.





The ac emitter resistance external to the transistor is

$$R_e = R_E \parallel R_L = 1.0 \text{ k}\Omega \parallel 1.0 \text{ k}\Omega = 500 \text{ }\Omega$$

The approximate resistance, looking in at the base, is

$$R_{in(base)} \cong \beta_{ac} R_e = (175)(500 \text{ }\Omega) = 87.5 \text{ k}\Omega$$

The total input resistance is

$$R_{in(tot)} = R_1 \parallel R_2 \parallel R_{in(base)} = 18 \text{ k}\Omega \parallel 18 \text{ k}\Omega \parallel 87.5 \text{ k}\Omega = \mathbf{8.16 \text{ k}\Omega}$$

The voltage gain is  $A_v \cong 1$ . By using  $r'_e$ , you can determine a more precise value of  $A_v$  if necessary.


$$V_E = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} - V_{BE} = (0.5)(10 \text{ V}) - 0.7 \text{ V} = 4.3 \text{ V}$$

Therefore,

$$I_E = \frac{V_E}{R_E} = \frac{4.3 \text{ V}}{1.0 \text{ k}\Omega} = 4.3 \text{ mA}$$

and
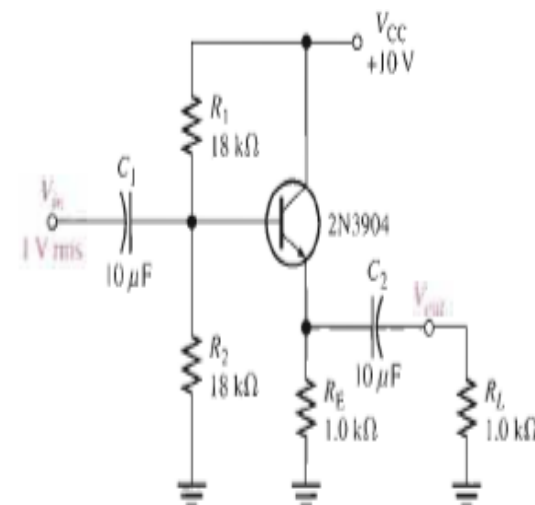
$$r'_e \cong \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{4.3 \text{ mA}} = 5.8 \text{ }\Omega$$



So,

$$A_v = \frac{R_e}{r'_e + R_e} = \frac{500 \, \Omega}{505.8 \, \Omega} = \mathbf{0.989}$$

The small difference in  $A_v$  as a result of considering  $r'_e$  is insignificant in most cases.

The overall current gain is  $A_i = I_e/I_{in}$ . The calculations are as follows:

$$I_e = \frac{V_e}{R_e} = \frac{A_v V_b}{R_e} \cong \frac{1 \, \text{V}}{500 \, \Omega} = 2 \, \text{mA}$$

$$I_{in} = \frac{V_{in}}{R_{in(\text{tot})}} = \frac{1 \, \text{V}}{8.16 \, \text{k}\Omega} = 123 \, \mu\text{A}$$

$$A_i = \frac{I_e}{I_{in}} = \frac{2 \, \text{mA}}{123 \, \mu\text{A}} = \mathbf{16.3}$$

The overall power gain is

$$A_p \cong A_i = 16.3$$

Since  $R_L = R_E$ , one-half of the total power is dissipated in  $R_L$ . Therefore, in terms of power to the load, the power gain is one-half of the overall power gain.

$$A_{p(\text{load})} = \frac{A_p}{2} = \frac{16.3}{2} = \mathbf{8.15}$$

